

A New Voltage Regulator Design

Linear voltage regulators have been commodity parts for many years and are often taken for granted as a DC power source. However, like any real device they have limitations. Using a better regulator can simplify circuit design, reduce component count and enhance performance. This article discusses the patented (U.S. Patent 8,294,440). design of a new high performance regulator and its benefits.

A Basic Feedback Voltage Regulator

The basic voltage regulator shown in figure 1 has a fixed reference voltage V_{REF} , an error amplifier A1 and an output transistor Q1. The error amplifier compares the output voltage to the reference voltage and makes them equal relative to the ratio of feedback resistors R1 and R2. V_{REF} current is set by current source Q3. In this particular variation, Q2 is also a current source and A1 controls the load current from Q1 by sinking any base current not needed to stimulate load current from the emitter.

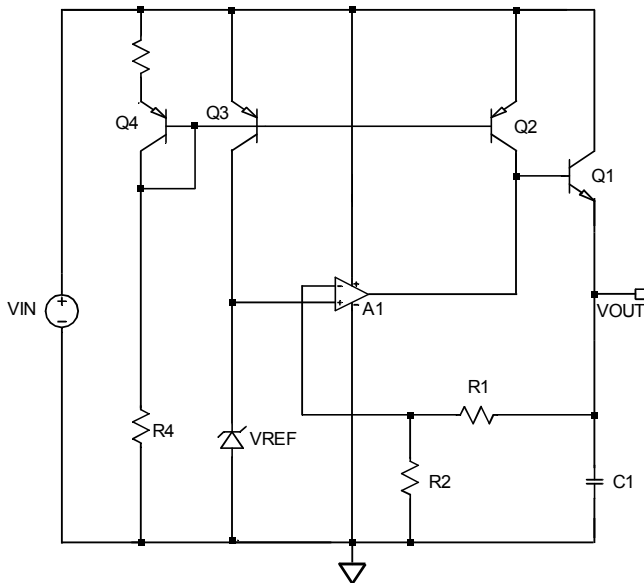


Figure 1: A basic voltage regulator topology

While this regulator is decent, it has multiple sources of error and some other limitations.

Error Sources

Power Supply Ripple Rejection of A1

First consider V_{IN} , which has noise that the regulator attempts to remove. Noise is defined here as any deviation from perfect DC: high frequency noise coupled from a power (mains) line; ripple from a filtered rectifier; digitally induced noise from nearby circuitry; traditional Johnson noise, etc.

A1 has its power source connected directly to the noisy input voltage and any non-DC signal on V_{IN} that eludes the supply rejection ability of A1 goes directly to V_{OUT} via the emitter follower Q1.

The simplest form of A1 is a resistively loaded common emitter inverter. This provides decent load regulation but poor supply rejection. A differential pair provides better rejection but still suffers from finite collector impedance and Early effect degradation. These regulators typically offer 40 to 80 dB of input AC rejection at low frequencies, which decreases as frequency goes up due to junction capacitance of Q1, Q2 and Q3 and coupling from the base of Q4.

Using an op amp for A1 gives much better supply rejection at low frequency, but the PSRR of most op amps is high (110dB) at DC and rolls off rapidly as frequency increases. Interestingly, our measurements show monolithic regulators' low frequency PSRR is generally not as good as that of a typical op amp, so either their internal amplifiers are not as good or other error sources dominate.

The Early effect of Q2 and Q3 collectors causes some modulation of their currents with V_{IN} changes. This appears at V_{OUT} as ripple that is not rejected.

Other Error Sources

When a changing load demands more or less current, V_{OUT} will change due to the low but finite impedance of Q1 emitter. A1 detects this difference and responds by changing Q1's base current to bring V_{OUT} back to its expected value. The bandwidth, loop stability and possibly the slew rate of A1 determine how fast the loop responds and V_{OUT} settles.

If $V_{OUT} = V_{REF}$, the loop gain of A1 is unity (R2 is infinite) and A1's bandwidth is maximized, assuming A1 is a transconductance amp. If $V_{OUT} > V_{REF}$, the

on Q1 and output current. While not as low as the V_{sat} of a single PNP pass device or the $V_{ds(on)}$ of a MOSFET, drop out voltage is quite low compared to many available regulators.

PSRR Measurements

With only two connections to VIN, it's clear there are fewer paths for unwanted input AC to get to VOUT, and the two connections are both high impedance—J1 drain and Q1 collector. This gives improved supply rejection compared to other available regulators as shown in figures 3 and 4, which show PSRR for a set of commercially available regulators.

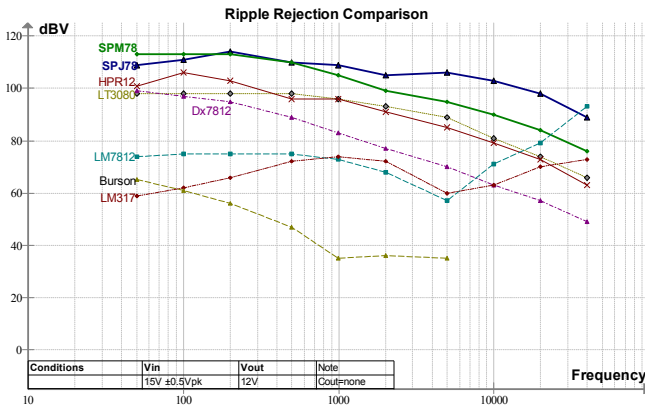


Figure 3: PSRR vs. frequency, 50Hz to 100KHz, Cout=None

Measurements for figure 3 were taken with no capacitor added to the regulator output, figure 4 measurements use a 100µF capacitor. All measurements were taken in the same test setup with the same equipment.

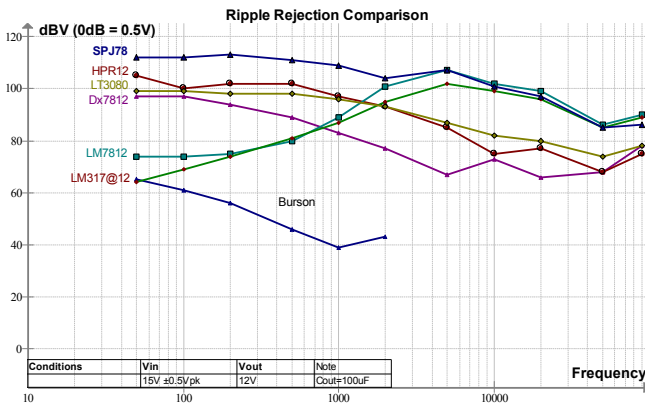


Figure 4: PSRR vs. frequency, 50Hz to 100KHz, Cout=100µF

Notice that the output capacitor greatly improves the supply rejection of monolithic regulators such as LM317 and LM7812 as frequency increases. Measurements used a capacitor at any adjust pin as specified by their respective data sheets.

Load Regulation

The extent to which a regulator can keep its output voltage constant with a changing load is its load regulation. DC or static load regulation is typically measured by monitoring Vout at two different DC load currents and taking their ratio. However, this measurement is not useful in a real world situation where the load can change by large relative amounts in a very short time. This type of AC load regulation is known as *load transient response* or dynamic performance. Dynamic performance is one of the most important and overlooked characteristics of a voltage regulator.

When an amplifier must supply a large fast current to a load, whether the load is a speaker, a capacitive cable or data converter, if the regulator output changes then transient response is compromised and the signal can be distorted. Not only will the part of the signal that caused the transient distortion be affected, but all signal components that exist while the regulator recovers will be affected.

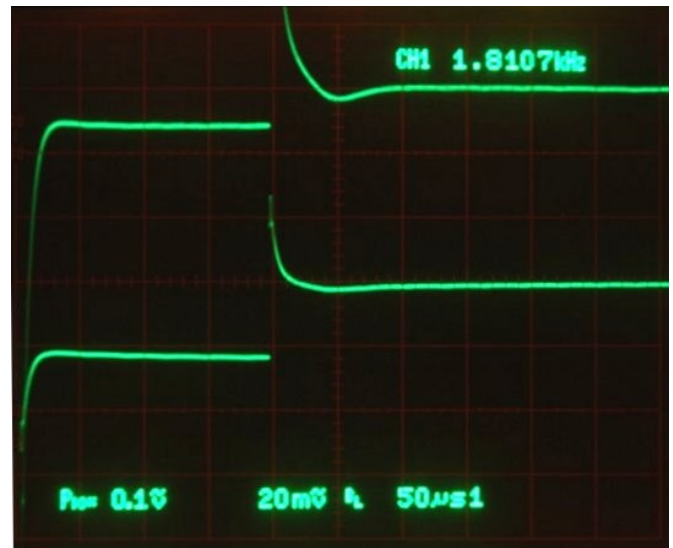


Figure 5: LM7812 load transient response, 1A current step.

Consider a standard monolithic voltage regulator such as the LM7812. When a 1 amp current pulse is demanded from the output, what happens? The oscillograph in figure 5 shows the output voltage (top trace) and the load current as 0.1V/0.1Ω per division (bottom trace).

The LT3080 output response is shown in figure 6, to illustrate a more recent (and award winning) design from Linear Technology.

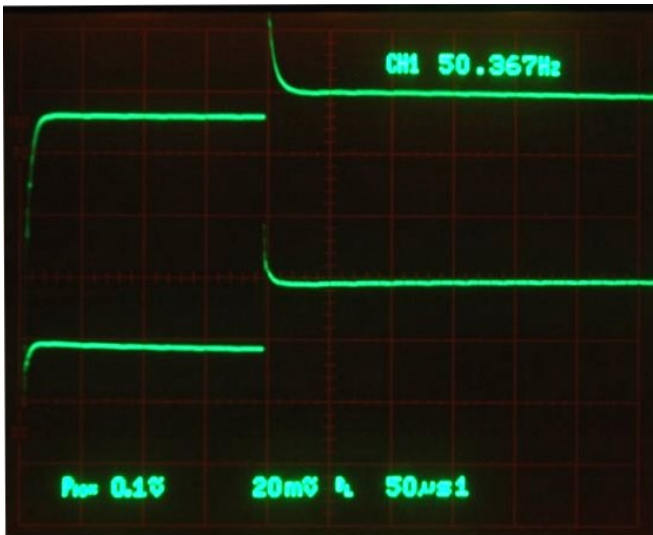


Figure 6: LT3080 load transient response, 1A current step.

This is a stringent test for a linear voltage regulator. It demonstrates how the regulator might respond to a load with digital circuitry such as a clock. A slow response may not cause a logic level error, but could increase clock jitter by delaying signal transitions. This is particularly critical in high resolution or high speed data converters and high data rate signal transceivers.

Contrast these results to the same test done on a Superpower in figure 7. Notice the exceptionally small transients when the current goes from 10mA to 1A and again when it goes from 1A back to 10mA.

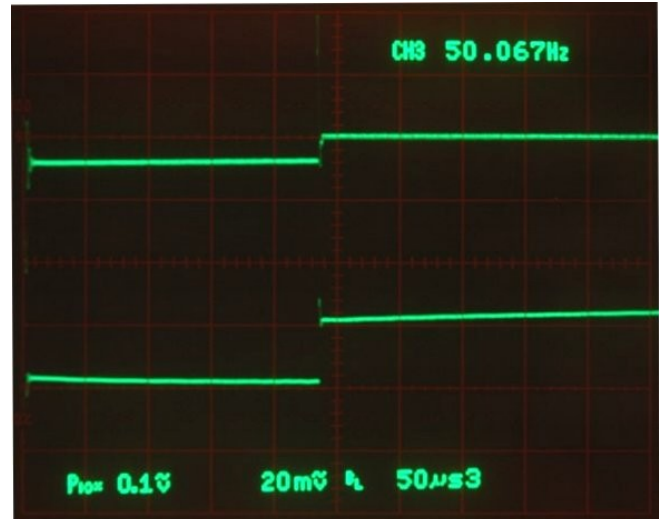


Figure 7: SP178 load transient response, 1A load current step.

Figure 8 shows the step response of a Belleson SPM78 12V regulator, which is a TO-220 size PCB that delivers up to 225mA. Note that all load transient step tests were done with a 100µF electrolytic capacitor at the regulator output.

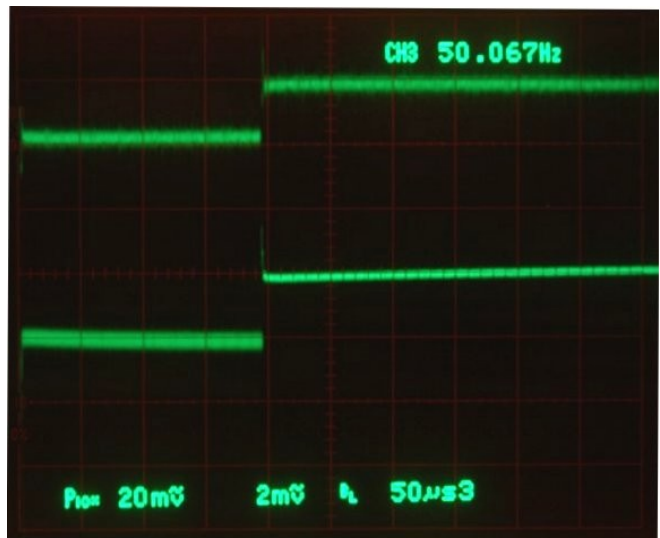


Figure 8: SPM78 load transient response, 200mA load current step.

Noise

The effect of power supply noise on a load circuit can be more or less depending on the circuit. To the extent that its differential halves match, a fully differential circuit cancels power supply noise by making it common to both halves. At the other extreme a single ended resistively loaded amplifier stage will pass power supply noise directly to the next stage.

It's easy to agree that low noise in a regulator is a worthy goal, and Superpower is one of the lowest noise voltage regulators available, with RMS noise of less than 1 PPM of V_{out} . SPJ measures $<10\mu V_{rms}$ (20Hz-20kHz) for a 12V output Superpower, making it ideal for use in low level subsystems such as microphone amplifiers, phono stages, preamplifiers, DACs, ADCs, digitizers, sensor amplifiers etc. The noise floor spectrum is shown in figure 8.

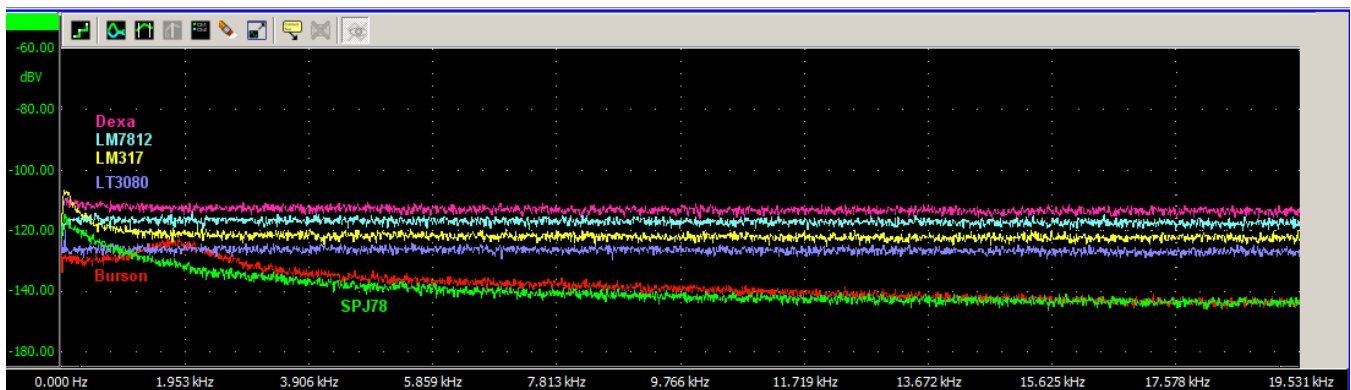


Figure 9: Noise measurement of several regulators

Conclusion

Standards for voltage regulator performance have been raised in a new regulator design from Belleson LLC. Belleson's patented Superpower voltage regulators offer the following benefits over others:

- Higher current
- Higher voltage
- Higher ripple rejection
- Faster transient step response
- Lower noise

If your requirements demand the very best performance, choose Superpower™.

Revised May 1, 2015
Copyright Belleson LLC
All rights reserved.
Superpower is a trademark of Belleson LLC.
All other names and brands are the property
of their respective owners.



<http://www.belleson.com/>